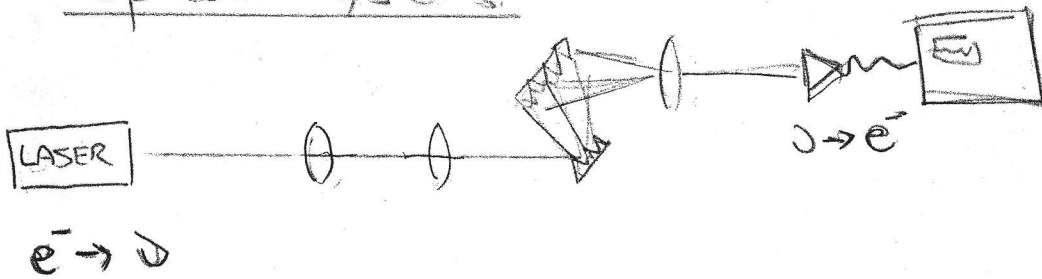


Optical Systems:



Until now we discussed mostly the J part of the set up. The rest of the course will be dedicated to the $J \rightarrow e^-$ and e^- part of the system. Sources (i.e. $e^- \rightarrow J$) part will not be discussed.

We will start with a review of basic (e^-) electronics building blocks. [A result of the previous course feedback]

Horowitz & Hill "The art of electronics"

Resistors:

Ohm's law $\Rightarrow V = IR$


highly linear $\Rightarrow \Delta R < 10^{-7} / 1 \text{ Volt}$
two "standard" kinds:

Carbon composition: $2.7 \Omega \leftrightarrow 22 M \Omega$

up to $2W$

Temp coeff: $10^{-3} / ^\circ C = \frac{\Delta R}{R}$

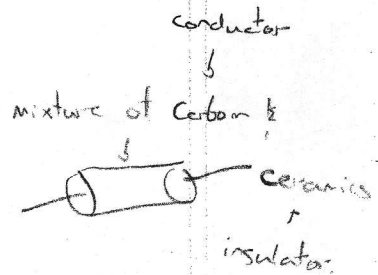
Tolerance: $10\% \sim 12 NIS$ $5\% \sim 5 NIS$




metal film: $10\ \Omega \leftrightarrow 200\ \text{m}\Omega$
 up to $2\ \text{W}$

Temp coeff: $\sim 5 \times 10^{-5} / ^\circ\text{C} = \frac{\Delta R}{R}$

Tolerance: $< 1\%$ 10-15 NIS

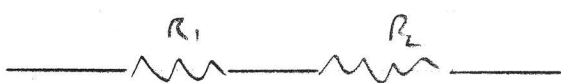


$$R = R_1 + R_2$$

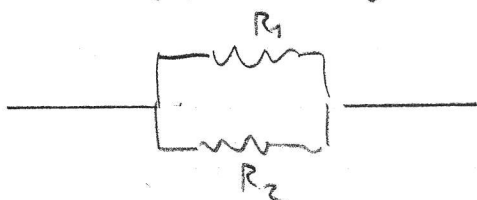

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Voltage divider:

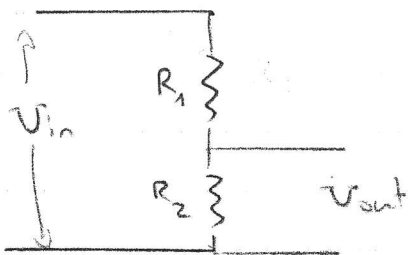

$$I = \frac{V_{in}}{R_1 + R_2}$$

$$\Rightarrow V_{out} = I R_2 = \frac{R_2}{R_1 + R_2} V_{in}$$


Voltage source: maintains fixed voltage regardless of load.

for AC sources matched to load. \Rightarrow transmission lines

A "real life" voltage source: Max $I \Rightarrow$ small series resistance.



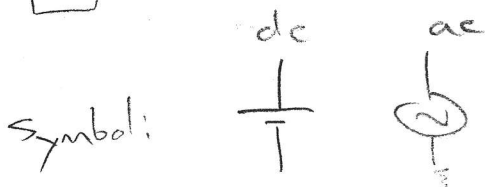alkaline battery: $I_{max} = 3\ \text{Amp}$ $3\ \Omega$ series resistance.




wants "open" circuit
 Meter to be short circuited

Current source: maintains a constant current regardless of load.

'real life' current sources have a max voltage they can supply.


Thevenin equiv. circuit:

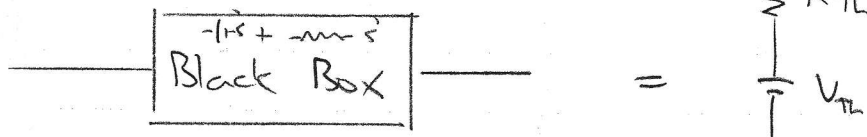

$$V_{TH} = V(\text{open circuit})$$

$$R_{TH} = \frac{V(\text{open circuit})}{I(\text{short circuit})}$$

Apply Thevenin to voltage divider:

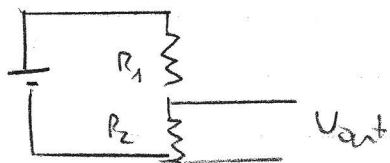

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{in}$$

$$R_{TH} = \frac{\frac{R_2}{R_1 + R_2} V_{in}}{V_{in} / R_1} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2} \quad \in \text{Parallel}$$

to make a voltage divider a good voltage source

$$\Rightarrow R_{TH} \rightarrow 0 \quad \Rightarrow R_1, R_2 \rightarrow 0 \quad \text{large constant current}$$