

## Electro-optics course, exercise # 5

### 1. Johnson-Nyquist noise in an Op-Amp circuit

Calculate the voltage RMS noise at the output of an inverting-amplifier op-amp circuit, due to Johnson-Nyquist noise in both its resistors:

